

SOLUTIONS MANUAL

POWER ELECTRONICS

CIRCUITS, DEVICES,
AND APPLICATIONS

THIRD EDITION

MUHAMMAD H. RASHID



Upper Saddle River, New Jersey 07458

CHAPTER 2

POWER SEMICONDUCTOR DIODES AND CIRCUITS

Problem 2-1

$t_{rr} = 5 \mu s$ and $di/dt = 80 A/\mu s$

(a) From Eq. (2-10),

$$Q_{RR} = 0.5 (di/dt) t_{rr}^2 = 0.5 \times 80 \times 5^2 \times 10^{-6} = 1000 \mu C$$

(b) From Eq. (2-11),

$$I_{RR} = \sqrt{2Q_{RR} \frac{di}{dt}} = \sqrt{2 \times 1000 \times 80} = 400 A$$

Problem 2-2

$V_T = 25.8 mV$, $V_{D1} = 1.0 V$ at $I_{D1} = 50 A$, and $V_{D2} = 1.5 V$ at $I_{D2} = 600 A$

Taking natural (base e) logarithm on both sides of Eq. (2-3),

$$\ln I_D = \ln I_S + \frac{v_D}{\eta V_T}$$

which, after simplification, gives the diode voltage V_D as

$$v_D = \eta V_T \ln \left(\frac{I_D}{I_S} \right)$$

If I_{D1} is the diode current corresponding to diode voltage V_{D1} , we get

$$V_{D1} = \eta V_T \ln \left(\frac{I_{D1}}{I_S} \right)$$

Similarly, if V_{D2} is the diode voltage corresponding to the diode current I_{D2} , we get

$$V_{D2} = \eta V_T \ln \left(\frac{I_{D2}}{I_S} \right)$$

Therefore, the difference in diode voltages can be expressed by

$$V_{D2} - V_{D1} = \eta V_T \ln\left(\frac{I_{D2}}{I_S}\right) - \eta V_T \ln\left(\frac{I_{D1}}{I_S}\right) = \eta V_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$

(a) For $V_{D2} = 1.5$ V, $V_{D1} = 1.0$ V, $I_{D2} = 600$ A, and $I_{D1} = 50$ A,

$$1.5 - 1.0 = \eta \times 0.0258 \times \ln\left(\frac{600}{50}\right), \text{ which give } \eta = 7.799$$

(b) For $V_{D1} = 1.0$ V, $I_{D1} = 50$ A, and $\eta = 7.999$

$$1.0 = 7.799 \times 0.0258 \ln\left(\frac{50}{I_S}\right), \text{ which gives } I_S = 0.347 \text{ A.}$$

Problem 2-3

$$V_{D1} = V_{D2} = 2000 \text{ V}, R_1 = 100 \text{ k}\Omega$$

(a) From Fig. P2-3, the leakage current are: $I_{S1} = 17$ mA and $I_{S2} = 25$ mA

$$I_{R1} = V_{D1}/R_1 = 2000/100000 = 20 \text{ mA}$$

(b) From Eq. (2-12), $I_{S1} + I_{R1} = I_{S2} + I_{R2}$

$$\text{or } 17 + 20 = 25 + I_{R2}, \text{ or } I_{R2} = 12 \text{ mA}$$

$$R_2 = 2000/12 \text{ mA} = 166.67 \text{ k}\Omega$$

Problem 2-4

For $V_D = 1.5$ V, Fig. P2-3 gives $I_{D1} = 140$ A and $I_{D2} = 50$ A

Problem 2-5

$$I_T = 200 \text{ A}, v = 2.5$$

$$I_1 = I_2, I_1 = I_T/2 = 200/2 = 100 \text{ A}$$

For $I_1 = 100$ A, Fig. P2-3 yields $V_{D1} = 1.1$ V and $V_{D2} = 1.95$ V

$$v = V_{D1} + I_1 R_1 \text{ or } 2.5 = 1.1 + 100 R_1 \text{ or } R_1 = 14 \text{ m}\Omega$$

$$v = V_{D2} + I_2 R_2 \text{ or } 2.5 = 1.95 + 100 R_2 \text{ or } R_2 = 5.5 \text{ m}\Omega$$

Problem 2-6

$$R_1 = R_2 = 10 \text{ k}\Omega, V_s = 5 \text{ kV}, I_{s1} = 25 \text{ mA}, I_{s2} = 40 \text{ mA}$$

$$\text{From Eq. (2-12), } I_{s1} + I_{R1} = I_{s2} + I_{R2}$$

$$\text{or } I_{s1} + V_{D1}/R_1 = I_{s2} + V_{D2}/R_2$$

$$25 \times 10^{-3} + V_{D1}/10000 = 40 \times 10^{-3} + V_{D2}/10000$$

$$V_{D1} + V_{D2} = V_s = 5000$$

$$\text{Solving for } V_{D1} \text{ and } V_{D2} \text{ gives } V_{D1} = 2575 \text{ V and } V_{D2} = 2425 \text{ V}$$

Problem 2-7

$$t_1 = 100 \text{ }\mu\text{s}, t_2 = 300 \text{ }\mu\text{s}, t_3 = 500 \text{ }\mu\text{s}, f = 250 \text{ Hz}, f_s = 250 \text{ Hz}, I_m = 500 \text{ A}$$

and $I_a = 200 \text{ A}$

$$(a) \text{ The average current is } I_{av} = 2I_m ft_1/\pi - I_a (t_3 - t_2)f = 7.96 - 10 = -2.04 \text{ A.}$$

$$(b) \text{ For sine wave, } I_{r1} = I_m \sqrt{ft_1/2} = 55.9 \text{ A and for a rectangular negative wave, } I_{r2} = I_a \sqrt{f(t_3 - t_2)} = 44.72 \text{ A}$$

$$\text{The rms current is } I_{rms} = \sqrt{55.9^2 + 44.72^2} = 71.59 \text{ A}$$

$$(c) \text{ The peak current varies from } 500 \text{ A to } -200 \text{ A.}$$

Problem 2-8

$$t_1 = 100 \text{ }\mu\text{s}, t_2 = 200 \text{ }\mu\text{s}, t_3 = 400 \text{ }\mu\text{s}, t_4 = 800 \text{ }\mu\text{s}, f = 250 \text{ Hz}, I_a = 150 \text{ A}, I_b = 100 \text{ A and } I_p = 300 \text{ A}$$

$$(a) \text{ The average current is}$$

$$I_{av} = I_a ft_3 + I_b f(t_5 - t_4) + 2(I_p - I_a) f(t_2 - t_1)/\pi = 15 + 5 + 2.387 = 22.387 \text{ A.}$$

$$(b) I_{r1} = (I_p - I_a) \sqrt{f(t_2 - t_1)/2} = 16.77 \text{ A,}$$

$$I_{r2} = I_a \sqrt{ft_3} = 47.43 \text{ A and } I_{r3} = I_b \sqrt{f(t_5 - t_4)} = 22.36 \text{ A}$$